

Introduction to Digital Logic



CS 64: Computer Organization and Design Logic
Lecture #11
Winter 2019



Ziad Matni, Ph.D.
Dept. of Computer Science, UCSB

Administrative



- Lab 5 this week
- You can review your midterm with a TA during office hours
 - *Last name: A thru L* **Bay-Yuan Hsu** **F 11 am – 1 pm**
 - *Last name: M thru Z* **Shiyu Ji** **F 3 pm – 5 pm**
 - If you can't go to these o/hs, you can see me instead, but let me know well-ahead of time first so I can get your exam from the TA...
- When reviewing your exams:
 - Do not take pictures, do not copy the questions
 - TA cannot change your grade
 - If you have a legitimate case for grade change, the prof. will decide
 - Legitimate = When we graded, we added the total points wrong
 - Not legitimate = Why did you take off N points on this question????

Lecture Outline

- Intro to Binary (Digital) Logic Gates
- Truth Table Construction
- Logic Functions and their Simplifications
- The Laws of Binary Logic

Digital i.e. Binary Logic

  - Electronic circuits when used in computers are a series of switches
- 2 possible states: either ON (1) and OFF (0)



- **Perfect for binary logic representation!**

Basic Building Blocks of Digital Logic

- Same as the bitwise operators:

NOT

AND


OR

XOR

etc...

- We often refer to these as “**logic gates**” in digital design


Electronic Circuit Logic Equivalents

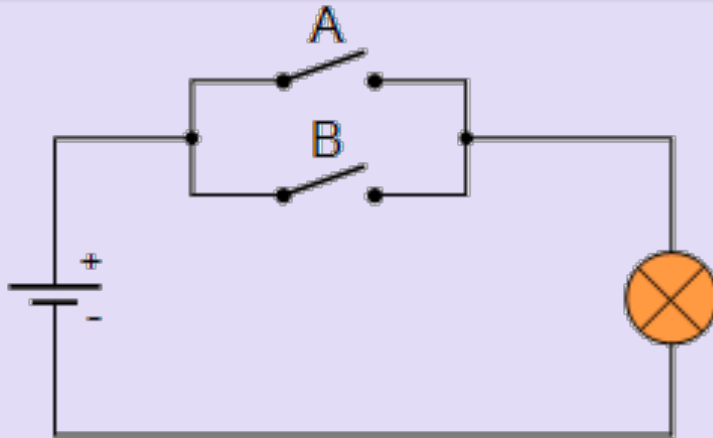

OR

Lamp - ON = "1"
Lamp - OFF = "0"

 Switch A - Open = "0", Closed = "1"
Switch B - Open = "0", Closed = "1"




AND

Lamp - ON = "1"
Lamp - OFF = "0"

Switch A - Open = "0", Closed = "1"
Switch B - Open = "0", Closed = "1"

Graphical Symbols and Truth Tables

NOT

 


A	\bar{A} or !A
0	1
1	0


Graphical Symbols and Truth Tables

AND and NAND

Practice Drawing
the Symbol!

 

A	B	A . B
0	0	0
0	1	0
1	0	0
1	1	1

 


A	B	$\overline{A . B}$ or $!(A.B)$
0	0	1
0	1	1
1	0	1
1	1	0


Graphical Symbols and Truth Tables

OR and NOR

Practice Drawing
the Symbol!

 

A	B	A + B
0	0	0
0	1	1
1	0	1
1	1	1

 


A	B	$\overline{A + B}$ or $\overline{!(A + B)}$
0	0	1
0	1	0
1	0	0
1	1	0

Graphical Symbols and Truth Tables

XOR and XNOR

Practice Drawing
the Symbol!

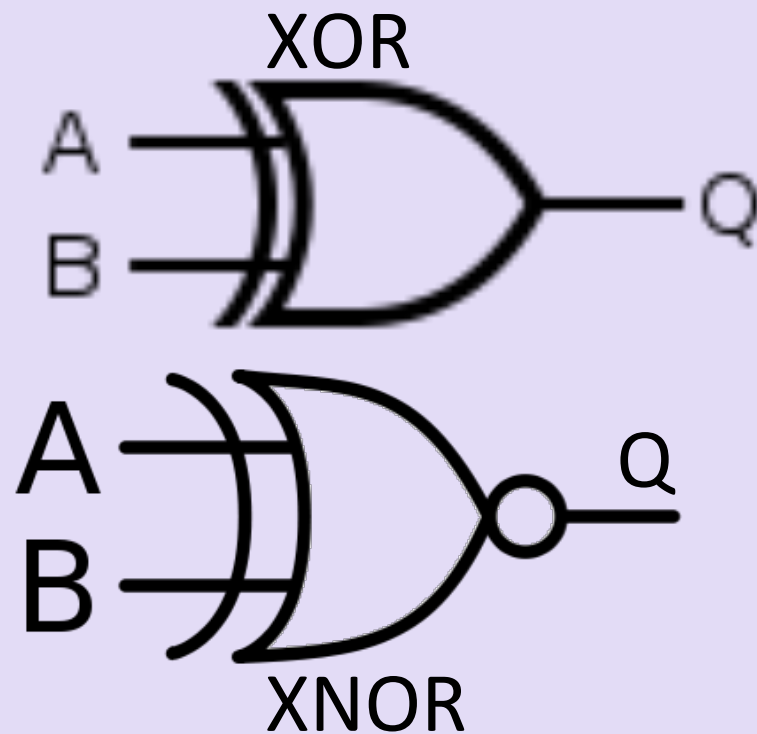


A	B	$A \oplus B$	$\overline{A \oplus B}$
0	0	0	1
0	1	1	0
1	0	1	0
1	1	0	1

Constructing Truth Tables

- T.Ts can be applied to ANY digital circuit
- They show ALL possible inputs with ALL possible outputs
- Number of entries in the T.T.
= 2^N , where N is the number of **inputs**

 Example: Constructing the T.T of a 1-bit Adder

- Recall the 1-bit adder:
 - Input1, Input2, and Carry-In
 - How many entries in the T.T. is that?
- **3 inputs:** I_1 and I_2 and C_I
 - Input1, Input2, and Carry-In
 - How many entries in the T.T. is that?
- **2 outputs:** R and C_O
 - Result, and Carry-Out
 - You can have multiple outputs: **each** will still depend on *some combination of the inputs*




Example: Constructing the T.T of a 1-bit Adder

T.T Construction Time!

Example: Constructing the T.T of a 1-bit Adder

#	<i>INPUTS</i>			<i>OUTPUTS</i>	
	I1	I2	CI	CO	R
0	0	0	0	0	0
1	0	0	1	0	1
2	0	1	0	0	1
3	0	1	1	1	0
4	1	0	0	0	1
5	1	0	1	1	0
6	1	1	0	1	0
7	1	1	1	1	1

 

Note the
order of the
inputs!!!

Logic Functions

- An **output function F** can be seen as a combination of 1 or more inputs
- Example:

$$F = A \cdot B + C \quad (\text{all single bits})$$

- This is called **combinatorial logic**

Equivalent in C/C++:

```
boolean f (boolean a, boolean b, boolean c)
{
    return ( (a & b) | c );
}
```

OR and AND as Sum and Product

- Logic functions are often expressed with basic logic building blocks, like ORs and ANDs and NOTs, etc...
- OR is sometimes referred to as “logical sum” or “logical union”
 - Partly why it’s symbolized as “+”
 - BUT IT’S **NOT** THE SAME AS NUMERICAL ADDITION!!!!!!
- AND as “logical product” or “logical disjunction”
 - Partly why it’s symbolized as “.”
 - BUT IT’S **NOT** THE SAME AS NUMERICAL MULTIPLICATION!!!!!!

Example

A	B	$A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

- **A XOR B** takes the value “1” (i.e. is TRUE) *if and only if*
 - $A = 0, B = 1$ i.e. $\neg A \cdot B$ is TRUE, or
 - $A = 1, B = 0$ i.e. $A \cdot \neg B$ is TRUE
- In other words, **A XOR B** is TRUE **iff** (if and only if) $A \cdot \neg B + \neg A \cdot B$ is TRUE


$$A \oplus B = \neg A \cdot B + A \cdot \neg B$$

Which can also be written as: $\bar{A} \cdot B + A \cdot \bar{B}$

Representing the Circuit Graphically

A	B	$A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0


$$A \oplus B = !A.B + A.!B$$

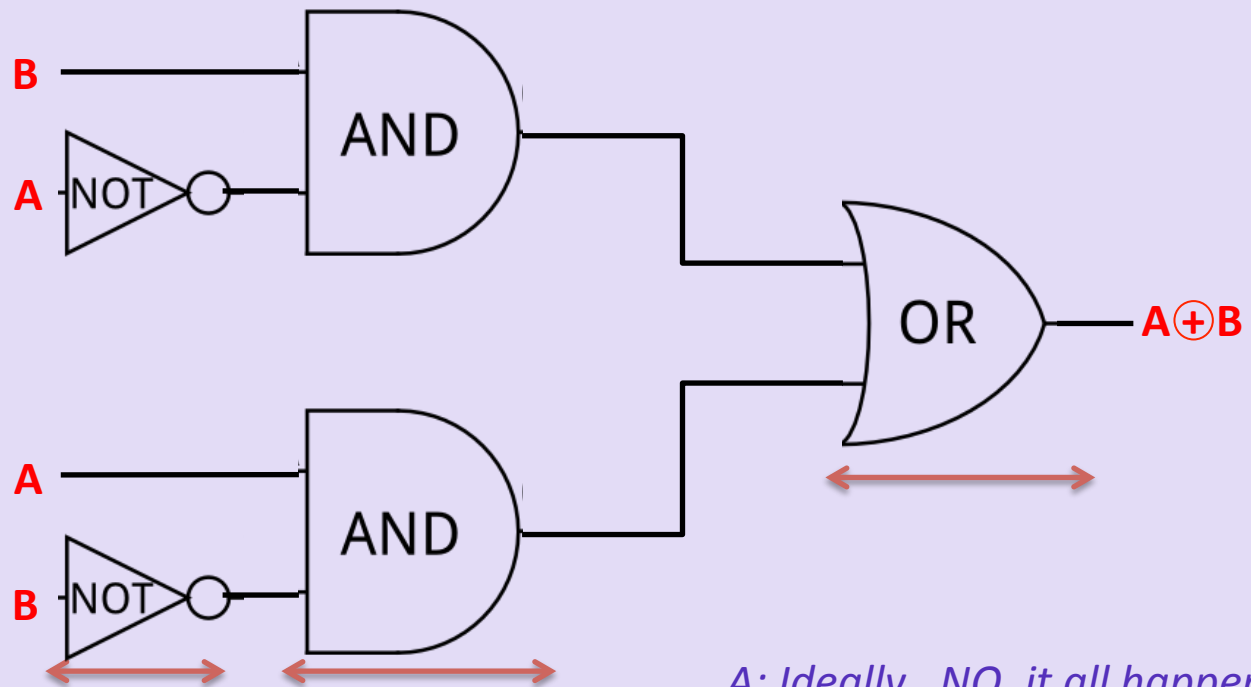

Q: Does it take any time for an electronic signal to go thru 3 "layers" of logic gates?

A: Ideally, NO, it all happens simultaneously.
In reality, OF COURSE it takes time (it's called **latency**)

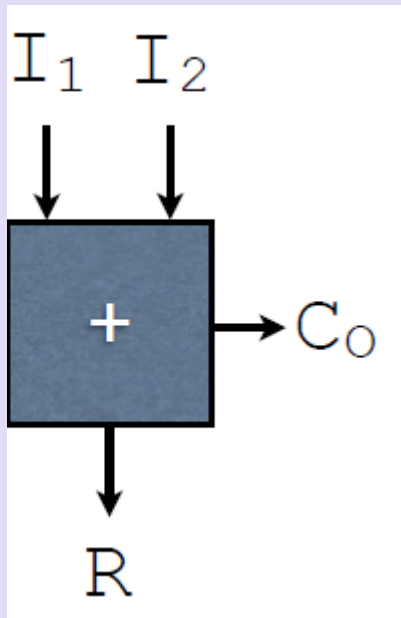What is The Logical Function for The Half Adder?



	INPUTS		OUTPUTS	
#	I1	I2	CO	R
0	0	0	0	0
1	0	1	0	1
2	1	0	0	1
3	1	1	1	0

Half Adder

1-bit adder that does not have a Carry-In (Ci) bit.

This logic block has only 2 1-bit inputs and 2 1-bit outputs

Our attempt to describe the outputs as functions of the inputs:

$$\begin{aligned} \text{CO} &= I_1 \cdot I_2 \\ \text{R} &= I_1 \oplus I_2 \end{aligned}$$

What is The Logical Function for A Full 1-bit adder?

#	INPUTS			OUTPUTS	
	I1	I2	CI	CO	R
0	0	0	0	0	0
1	0	0	1	0	1
2	0	1	0	0	1
3	0	1	1	1	0
4	1	0	0	0	1
5	1	0	1	1	0
6	1	1	0	1	0
7	1	1	1	1	1

Ans.:

$$CO = \neg I1.I2.CI + I1.\neg I2.CI + I1.I2.\neg CI + I1.I2.CI$$

$$R = \neg I1.\neg I2.CI + \neg I1.I2.\neg CI + I1.\neg I2.\neg CI + I1.I2.CI$$

Minimization of Binary Logic

- Why?
 - It's MUCH easier to read and understand...
 - Saves memory (software) and/or physical space (hardware)
 - Runs faster / performs better
 - Why?... remember *latency*?
- For example, when we do the T.T. for (see demo on board):
$$X = A.B + A.!B + B.!A$$
, we find that it is the same as
$$\mathbf{A + B}$$

(saved ourselves a bunch of logic gates!)

Using T.Ts vs. Using Logic Rules

- In an effort to simplify a logic function, we don't always have to use T.Ts – we can use *logic rules* instead

Example: What are the following logic outcomes?

$$A \cdot A \quad A$$

$$A + A \quad A$$

$$A \cdot 1 \quad A$$

$$A + 1 \quad 1$$

$$A \cdot 0 \quad 0$$

$$A + 0 \quad A$$

Using T.Ts vs. Using Logic Rules

- Binary Logic works in **Associative** ways
 - $(A.B).C$ is the same as $A.(B.C)$
 - $(A+B)+C$ is the same as $A+(B+C)$
- It also works in **Distributive** ways
 - $(A + B).C$ is the same as: **$A.C + B.C$**
 - $(A + B).(A + C)$ is the same as:
 - $A.A + A.C + B.A + B.C$**
 - $= A + A.C + A.B + B.C$**
 - $= A + B.C$**

More Examples of Minimization *a.k.a Simplification*

- Simplify:
$$\begin{aligned} R &= A.B + !A.B \\ &= (A + !A).B \\ &= B \end{aligned}$$

Let's verify it with a truth-table

Note: often, the AND dot symbol (.) is omitted, but understood to be there (like with multiplication dot symbol)

- Simplify:
$$\begin{aligned} R &= !ABCD + ABCD + !AB!CD + AB!CD \\ &= BCD(A + !A) + !AB!CD + AB!CD \\ &= BCD + B!CD(!A + A) \\ &= BCD + B!CD \\ &= BD(C + !C) \\ &= BD \end{aligned}$$

Let's verify it with a truth-table

More *Simplification* Exercises

- Simplify:
$$\begin{aligned} R &= !A!BC + !A!B!C + !ABC + !AB!C + A!BC \\ &= !A!B(C + !C) + !AB(C + !C) + A!BC \\ &= !A!B + !AB + A!BC \\ &= !A(!B + B) + A!BC \\ &= !A + A!BC \end{aligned}$$

You can verify it with a truth-table

- Reformulate using **only** AND and NOT logic:

$$\begin{aligned} R &= !AC + !BC \\ &= C(!A + !B) \\ &= C. !(A.B) \quad \leftarrow \text{De Morgan's Law} \end{aligned}$$

Important: Laws of Binary Logic

Circuit Equivalence - each law has 2 forms that are duals of each other.

Name	AND form	OR form
Identity law	$1A = A$	$0 + A = A$
Null law	$0A = 0$	$1 + A = 1$
Idempotent law	$AA = A$	$A + A = A$
Inverse law	$A\bar{A} = 0$	$A + \bar{A} = 1$
Commutative law	$AB = BA$	$A + B = B + A$
Associative law	$(AB)C = A(BC)$	$(A + B) + C = A + (B + C)$
Distributive law	$A + BC = (A + B)(A + C)$	$A(B + C) = AB + AC$
Absorption law	$A(A + B) = A$	$A + AB = A$
De Morgan's law	$\overline{AB} = \bar{A} + \bar{B}$	$\overline{A + B} = \bar{A}\bar{B}$

Your To-Dos

- Review this material!
- Lab #5 is due on **Wednesday**

</LECTURE>